Given the following RISC-V instruction and register / data memory values, show the propagation of signals through the reduced Single-Cycle datapath that calculate the result of the instruction. You are permitted and encouraged to refer to the RISC-V Green sheet while completing the problem. The values of the registers / memory are the values at the beginning of the instruction.

- PC: 0x7fffff100 5 rsl rs? Instruction: add x18, x19, x20 6 rd=rsl+rs2
- Register x18 contains 0x0000002A
- Register x19 contains 0x00000014

Register x20 contains 0x00000007

0000000 | 10010 | 10011 | 000 | 10100 | 0110011

